



LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034

B.Sc. DEGREE EXAMINATION – PHYSICS

FOURTH SEMESTER – APRIL 2015

PH 4506 - ELECTRONICS - I

Date : 16/04/2015
Time : 09:00-12:00

Dept. No.

Max. : 100 Marks

PART – A

Answer ALL Questions:

(10 x 2 = 20 marks)


1. State Norton's Theorem.
2. Define a linear circuit.
3. Explain d.c. load line.
4. Determine the operating frequency of a Colpitt's oscillator given $C_1=0.001\mu\text{F}$, $C_2=0.01\mu\text{F}$ and $L=15\text{mH}$.
5. State two characteristic feature of an ideal op-amp.
6. Define CMRR and express it in decibels.
7. Simplify the Boolean expression, $Y = (A+B+C).(A+B)$.
8. Draw the logic symbol and write the truth table of a D flip-flop.
9. State any two advantages of Integrated Circuits.
10. Write the four basic types of constructions employed in the manufacture of IC.

PART – B

Answer ANY FOUR Questions:

(4 x 7.5 = 30 marks)

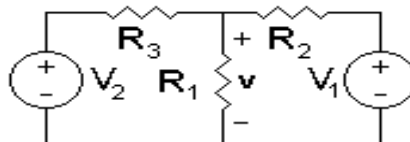11. State superposition theorem and use it to find the current through R_1 in the following circuit where $V_2=10\text{V}$; $V_1=5\text{V}$; $R_1=1\Omega$; $R_2= 3\Omega$; $R_3=2\Omega$. (1.5+6)



12. Explain with a neat circuit the voltage divider biasing technique. (7.5)
13. Describe the construction and working of an n-channel JFET (2.5+5)
14. Design a 4-to-1 multiplexer and explain its operation with the relevant function table. (7.5)
15. Write short note on memory devices ROM and RAM. (4.5+3)
16. Explain the fabrication of monolithic Integrated Circuits. (7.5)

PART C

Answer ANY FOUR questions:

(4 x 12.5 = 50 marks)

17. Obtain expressions for A_i , A_v and Z_i in terms of 'h' parameters for a transistor amplifier connected in common emitter configuration with necessary equivalent circuit. (3.5+9)
18. Explain with a neat circuit the functioning of an RC coupled amplifier. Discuss its frequency response curve. (12.5)
19. (a) Describe with a circuit diagram the functioning of an op-amp as a summing amplifier.
- (b) Explain the functioning of SCR as a switch. (6.5+6)
20. (a) Explain the working of a JK flip flop with the logic diagram and truth table.
- (b) Draw the logic circuit and explain the working of a 3 bit binary ripple counter with the relevant truth table. (6.5+6)
21. With a neat circuit explain the working of a transistor Astable Multivibrator. (12.5)
22. Explain with necessary diagrams the fabrication of transistor and resistor on monolithic Integrated Circuits. (6.5+6)

\$\$\$\$\$\$