

**LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034**

**B.Sc. DEGREE EXAMINATION – PHYSICS**

**THIRD SEMESTER – November 2009**

**PH 3504/PH 3502 - ELECTRONICS - I**

Date & Time: 04/11/2009 / 9:00 - 12:00 Dept. No.

Max. : 100 Marks

**PART A**

**Answer ALL questions:**

**10 x 2 = 20 marks**

1. Convert a constant current source producing 6 mA across  $2k\Omega$  into an equivalent voltage source.
2. List any two limitations of h parameters.
3. Draw the dc Load line for a CE type transistor amplifier with  $V_{CC}=12v$  and  $R_C=2K\Omega$ .
4. State the necessity for an Amplifier in an Oscillator circuit.
5. List the two basic characteristics of an ideal Opamp.
6. Determine the values of  $R_{B1}$  and  $R_{B2}$  of a UJT which has the intrinsic stand-off ratio = 0.6 & inter-base resistance =  $10k\Omega$ .
7. What is a 'Redundant Group' in a K map ? What is its effect?
8. What is a Multiplexer ?
9. How many flip flops are required to store  $2009_{10}$  in a binary register.
10. What is the modulus of a (i) 3BIT ripple counter & ii) 3BIT ring counter ?

**PART B**

**Answer ANY FOUR questions:**

**4 x 7.5 = 30 marks**

11. Derive the condition for maximum power transfer from a source to a load.
12. Explain the need for biasing and any one method of biasing a transistor.
13. Explain how the gate loses control once the SCR is triggered ON.
14. Describe the logic circuit of a M/S- JK Flip Flop and explain its working.
15. List the differences between Static RAM & Dynamic RAM.  
Explain any one application of ROM.

**PART C**

**Answer ANY FOUR questions:**

**4 x 12.5 = 50 marks**

16. Find the h parameters of the circuit given below:  
CIRCUIT
17. Draw Wien's bridge oscillator circuit using Transistor and explain its working.
18. Explain the mechanism of current conduction in a MOSFET.
19. Explain Add/Sub operations of 4-bit Parallel Binary Adder circuit with examples.
20. Draw a 3-Bit Johnson's Shift counter using JK flip flops and describe the sequence of operations. List the two illegal states of the counter.

\*\*\*\*\*