

**LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034****B.Sc. DEGREE EXAMINATION – PHYSICS****FIFTH SEMESTER – APRIL 2023****UPH 5601 – ELECTRONICS - II**

Date: 15-05-2023

Dept. No. 

Max. : 100 Marks

Time: 01:00 PM - 04:00 PM

**PART – A****(10x 2 = 20 Marks)****Answer ALL questions**

- |    |  |
|----|--|
| 1  | Differentiate between analog and digital signals.  |
| 2  | Find the accuracy of a D/A converter if the theoretical output voltage is 10 volts and the actual output voltage lies between 9.9 volts and 10.1 volts |
| 3  | What is phase locked loop?   |
| 4  | Draw the circuit diagram of IC 555 as a Schmitt trigger.   |
| 5  | If the 8085 adds 85H and 1EH, specify the contents of the accumulator and the status of the S, Z, and AC flags?  |
| 6  | Why is the data bus bi-directional?  |
| 7  | Assume that the accumulator contains 6CH and register D contains 2EH. Write an asm program to add these two numbers in immediate mode of addressing.   |
| 8  | Write an asm program to store the data 32H in ACC into the memory location 4000H.  |
| 9  | What are the types of interfacing in microprocessor 8085?  |
| 10 | Write the features of 8255 A.  |

**PART – B****Answer any four questions****(4 x 7.5 = 30 Marks)**

- |    |  |
|----|--|
| 11 | With a neat diagram, explain the working of an op- amp as an integrator.   |
| 12 | Explain the working of an astable multivibrator using IC 555 timer.  |
| 13 | Elucidate the significance of LOGIC and BRANCHING instructions of 8085 $\mu$ P with two examples.  |
| 14 | Write an asm program to multiply two 8-bit numbers 03H and 1B H stored in memory locations 2200H and 2201H by repetitive addition and store the result in memory locations 2300H. (Show the multiplication and the result) |
| 15 | Explain the three different operating modes of 8255 A.   |
| 16 | With a neat diagram, explain the working of a counter type A/D converter.  |

**PART – C****Answer any four questions****(4 X 12.5 =50 Marks)**

- |    |  |
|----|--|
| 17 | <p>(a) Explain with circuit, the working of a 4-bit R-2R ladder D/A converter using Op –amp. <b>(9 marks)</b></p> <p>(b) What will be the output voltage of a 4-bit R-2R ladder corresponding to the binary inputs (a) 1000 (b) 1100 (c) 0110? Given logic 0 corresponds to 0 volt and 1 corresponds to 16 volts. <b>(3.5 marks)</b></p> |
| 18 | With a neat circuit diagram, discuss the working of a monostable multivibrator using operational amplifier. Derive the expression for pulse width.   |

19	Explain in detail the internal architecture of microprocessor 8085 with a neat block diagram.
20	(a) Write an assembly language program to divide two 8-bit numbers in direct mode of addressing. (b) Write an assembly language program to find the largest among 10 numbers in an array. <b>(5 +7.5 marks)</b>
21	Draw the pin configuration of IC 555 timer. With a neat diagram, explain its internal architecture and working
22	With a neat diagram, explain the working of programmable peripheral interface 8255 A.

#####