



Date: 13-11-2024

Dept. No.

Max. : 100 Marks

Time: 09:00 am-12:00 pm

SECTION A - K1 & K2 (CO1)

Q.No	Levels	Answer ALL the Questions	(10 x 2 = 20)
1	K1	What are Don't care conditions in Simplification?	
2		Define adders.	
3		Define flip-flop.	
4		Mention the applications of shift register.	
5		Find the given binary number (100110) to grey code.	
6	K2	Demonstrate the arithmetic addition 1001+10101+1111.	
7		Summarize instruction Codes in computer organization.	
8		Explain common bus system.	
9		Outline the arithmetic instructions.	
10		Show the components of CPU.	

SECTION B – K3 & K4 (CO2)

		Answer ALL the Questions	(4 x 10 = 40)
11	K3	Solve using Map method for the given Function. a. $F(X,Y,Z)=\sum(1,3,5,7)$ b. $F(A,B,C)=\pi(0,2,4,6)$	
12		[OR]	
13		Construct the various logic gates with truth tables and explain.	
14		Construct SISO and PISO and explain.	
15		[OR]	
16	K4	Identify and explain the working of multiplexer and demultiplexer in detail.	
17		Analyze and convert the following a. Decimal $(7894)_{10}$ to Octal. b. Octal $(453)_8$ to Hexadecimal.	
18		[OR]	
		Inference error detection method with an example.	
		Distinguish the various computer registers in computer organization.	
		[OR]	
		Examine Logical and bit Manipulation instruction with examples.	

SECTION C – K5 & K6 (CO3)

Answer ALL the Questions			(2 x 20 = 40)
19	K5	A. Explain the working of JK flip flop. B. Explain encoders with a neat diagram and truth table.	(10) (10)
20		Evaluate the following a. Perform subtraction 10111 -1010 using 1's and 2's complement b. Perform subtraction 1011 -1000 using 1's and 2's complement c. Perform Addition 1010 and -1001 using 1's and 2's complement d. Perform Addition 0111 and -1000 using 1's and 2's complement	[OR]
21	K6	A. Discuss about Addressing modes. B. Elaborate Instruction format in detail.	(10) (10)
22		Design a block diagram of general register organization explain its working.	[OR]
