



Date: 13-11-2024

 Dept. No.

Max. : 100 Marks

Time: 09:00 am-12:00 pm

SECTION A - K1& K2 (CO1)

Q.No	Levels	Answer ALL the Questions	(10 x 2 = 20)
1	K1	Find the decimal equivalent of binary numbers 100101 and 110110.	
2		What is Hexadecimal Number system?	
3		What is meant by logic gate?	
4		What is Karnaugh map?	
5		Find the 2's complement of binary number $(1011\ 1110)_2$	
6	K2	Draw the circuit of Half Adder.	
7		Give the use of flip flop. Which flip flop is mostly used?	
8		What is D- flip flop?	
9		Define Multiplexer.	
10		What is meant by decoder?	

SECTION B– K3& K4 (CO2)

		Answer ALL the Questions	(4 x 10 = 40)
11	K3	Convert the following numbers: a. $(19.625)_{10}$ to binary b. $(3FC.8)_H$ to decimal c. $(65,534)_{10}$ to hex equivalent d. $(41)_8$ to a binary e. $(105)_H$ to octal	[OR]
12		Explain the laws of Boolean Algebra. Prove that $(A + C)(AD + A\bar{D}) + AC + C = A+C$ and $A+CB = (A+B)(A+C)$	
13		Discuss the function of Controlled inverter with suitable circuit.	[OR]
14		Describe J-K Master slave flip flop. What are its advantages and disadvantages?	
15		Explain the action of decimal to BCD encoder.	[OR]
16	K4	Explain the following with reference to K-map: a) Pairs Quads and Octets	

	b) Don't care conditions c) Simplify using K - map $Y = F(A,B,C,D) = \sum (1,3,7,11,15) + \sum d(0,2,5,8)$
--	---

17	Add the following binary numbers (a) $(1011)_2$ and $(1001)_2$ (b) $(1110)_2$ and $(1010)_2$ (c) $(1110110)_2$ and $(1100110)_2$ (d) $(101010)_2$ and $(011011)_2$ [OR]
18	Explain the working of BCD to seven segment decoder.

SECTION C – K5 & K6 (CO3)

	Answer ALL the Questions	(2 x 20 = 40)
19	K5	Explain basic logic gates with suitable diagram and truth table. Show that NAND and NOR are Universal logic gates [OR]
20		a) State the rules for binary subtraction. Discuss 1' complement and 2' complement method with examples. b) Describe the function of a Full Adder and obtain expressions for SUM and CARRY outputs
21	K6	With a neat circuit diagram explain the working of a RS flip-flop. State the difference between RS flip-flop and D flip-flop. [OR]
22		Explain the working of 1 to 4 demultiplexer. What are the differences between multiplexer and demultiplexer.

\$\$\$\$\$\$\$\$\$\$\$\$\$\$\$\$