

**LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034**



**B.Sc. DEGREE EXAMINATION – PHYSICS**

**THIRD & FIFTH SEMESTER – APRIL 2018**

**PH 3504 / PH 3502 / PH 5501– ELECTRONICS - I**

Date: 05-05-2018  
Time: 01:00-04:00

Dept. No.

Max. : 100 Marks

**PART-A**

**(10x2=20 Marks)**

**Answer ALL the questions**

1. State Thevenin's Theorem.
2. What is a constant voltage source?
3. Write the different methods of transistor biasing.
4. What is a monostable multivibrator?
5. Draw the equivalent circuit of UJT.
6. A difference amplifier has a differential voltage gain of 2000 and a common mode gain of 0.2. Calculate CMRR and write it in dB.
7. What is the function of a multiplexer?
8. Draw the logic diagram and write the truth table of a D - flip-flop.
9. What is a ripple counter?
10. Write any two differences between ROM and RAM.

**PART-B**

**(4x7.5=30 Marks)**

**Answer Any Four questions**

11. State the maximum power theorem and derive the condition for transfer of maximum power from source to a load. **(2.0 + 5.5)**
- 12.(a) Explain the working of a phase shift oscillator with a neat circuit diagram. **(5.0)**  
(b) A phase shift oscillator uses 5pF capacitors. Find the value of R to produce a frequency of 800 kHz. **(2.5)**
13. With relevant circuit diagrams, explain the operation of OP-AMP as summing and difference amplifier. **(3.5+4.0)**
14. Describe the function of a 7 segment decoder with a neat diagram. **(7.5)**
15. Explain the working of three bit binary ripple counter using JK flip flop. **(7.5)**

**PART-C**

**Answer Any Four questions**

**(4x12.5=50)**

16. Obtain expressions for the input impedance, current gain, voltage gain and output impedance in terms of h-parameters using the equivalent circuit of a transistor in CE configuration.

17. With necessary circuit explain the construction and working of a Bistable multivibrator. **(5.0+7.5)**

18. Describe the construction and working of a silicon controlled rectifier. With circuit diagram, explain how it acts as a half wave rectifier. **(7.5+5.0)**

19. Explain the operation of JK flip - flop and JK Master Slave flip-flop with their logic diagrams and truth tables. **(6.5+6.0)**

20) With neat circuit diagrams, explain the function of (a) shift left and (b) shift right shift registers. **(6.5+6.0)**

\*\*\*\*\*