



LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034

B.Sc. DEGREE EXAMINATION – COMPUTER SCIENCE

THIRD SEMESTER – NOVEMBER 2017

PH 3106 – APPLIED ELECTRONICS

Date: 09-11-2017

Dept. No.

Max. : 100 Marks

Time: 09:00-12:00

PART A

ANSWER ALL QUESTIONS

(10×2=20)

1. What is zener diode?
2. Write two characteristics of an ideal operational amplifier?
3. What is doping in extrinsic semiconductor?
4. Simplify $\bar{A}(A+B)$ using Boolean identities.
5. What is a half subtractor?
6. Simplify using K-map = $F(A,B,C) = (0,2,4,6,7)$.
7. What is virtual memory?
8. Draw the circuit diagram of a three bit ring counter.
9. List the various computer registers.
10. Draw the block diagram of 'D' flip flop using JK flip flop and give its truth table.

PART B

ANSWER ANY FOUR QUESTIONS

(4×7.5=30)

11. Explain the different types of semiconductor.
12. Explain the working of a summing amplifier with neat diagram.
13. What is a decoder? Explain 3-8 decoder with a neat diagram.
14. Explain the working of clocked RS flip-flop and give its truth table.
15. Draw the block diagram and explain the various components in memory hierarchy.

PART C

ANSWER ANY FOUR QUESTIONS

(4×12.5=50)

16. Explain the mechanism of current conduction in metals and hence derive the expression for the total current density.
17. Explain the working of an op-amp based 4 bit R-2R ladder D/A convertor with diagram.
18. (a) State and prove Demorgan's theorem. (6 marks)
(b) Show how NAND gate is an universal gate. (6.5 marks)
19. (a) Explain the shift left shift register with a neat diagram. (6 marks)
(b) Briefly explain the working of a D-flip flop with its truth table. (6.5 marks)
20. (a) Discuss in detail about timing and control in a digital computer. (7 marks)
(b) Write short notes on RAM and ROM.
